

## Using a BS-1 PCB for driving 2-4 color signals.

### ***Build instructions***

1. Place 2 wires on the PCB. They are colored red on the image to the right.
2. Place the following parts:
  1. U1
  2. R2..R5
  3. C1
3. Connect 4 wires from the PCB to an MGV50 (or connector). They are colored blue on the image to the right.
4. Connect the signal to the PCB. They connections are colored orange.

